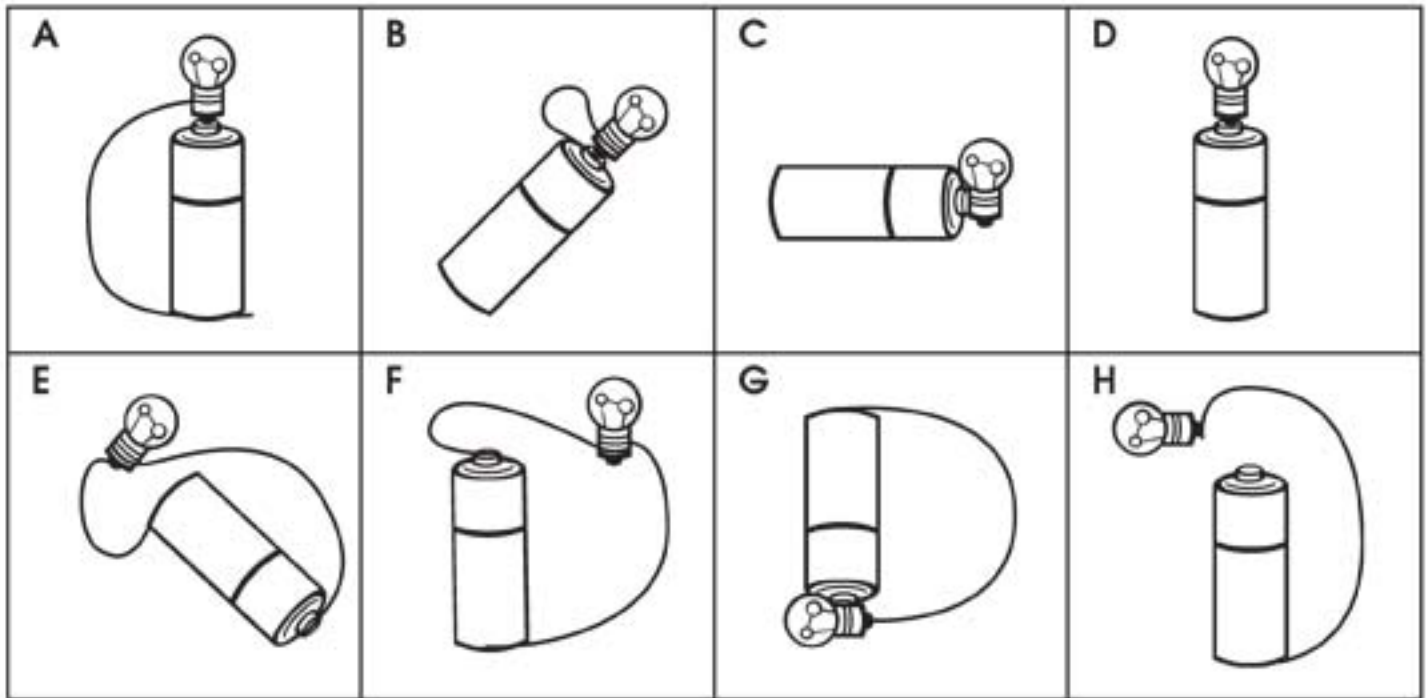


Making Circuits Work

Make each of the circuits below with your group, and find out if they work. Record what you find out in the table. Can you explain why some of the circuits work and some do not?



Circuit	Does the circuit work? (Yes/No)	Why?	Circuit	Does the circuit work? (Yes/No)	Why?
A			E		
B			F		
C			G		
D			H		